

## ZNR Application Note


### General Inductive Load

#### 1. Industry Segments:

**Field of Industry:** Inductive devices

**Product:** Relay coil, Electric magnet, Solenoid, Motor, Transformer, Inductive actuator, Magnetic contactor, etc.
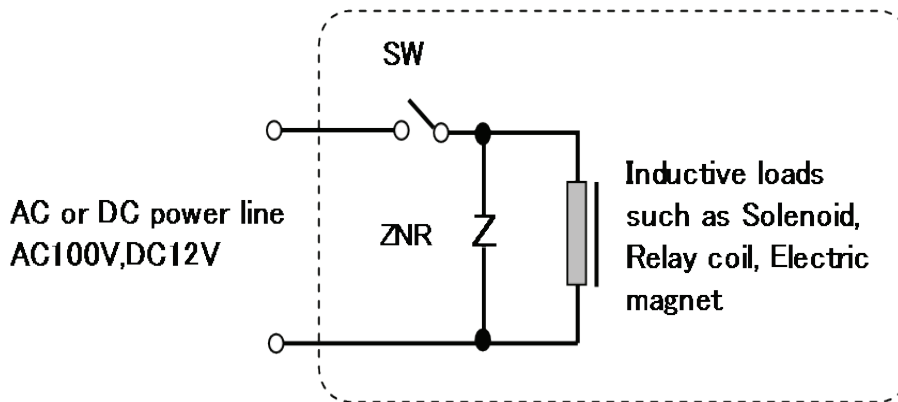
#### 2. Transient Surge Voltage and its Protection by Using ZNR:



#### Aim of ZNR Application:

Suppression of switching surge voltage from the inductor

#### Problems with Surge Voltage:

**Kind of surge voltage:** Switching surge voltage

**Path of surge voltage:** Power line connected to Inductive loads

**Failed parts or circuits:** Malfunction of the electronic circuits connected to the same power line

#### How to Apply ZNR to Circuit: (Blue Part Numbers Indicate NEW "E-Series")

**Connection:** Power line of inductive loads(line-line forming loop circuit)

#### ZNR part number selection (representative):

For AC100V : ERZE A271, For AC200V :ERZE A471, For DC12V : ERZV D220

is a nominal disc size of ZNR and should be selected by an inductive load energy etc.

#### Precaution in surge protection designing (Parameters to be considered for ZNR selection):

Maximum power line voltage, current into inductive load, switching repetition and their interval should be taken into account.

#### 3. More Information:

Home page for up-to-date information: <http://na.industrial.panasonic.com/products/circuit-thermal-protection/circuit-protection/znr-transientsurge-absorbers>